



# **Chittagong University of Engineering and Technology**

## **Department of Electronics and Telecommunication Engineering**

VLSI Technology Sessional

ETE 404

Lab Project

---

**8x1 MUX schematic, ADE simulations, Power usage, Symbol and Stick Diagram**

---

Name: Isfar Nayen


ID: 1908023

Level: 04

Term: 01


Group: 01

## Schematic:

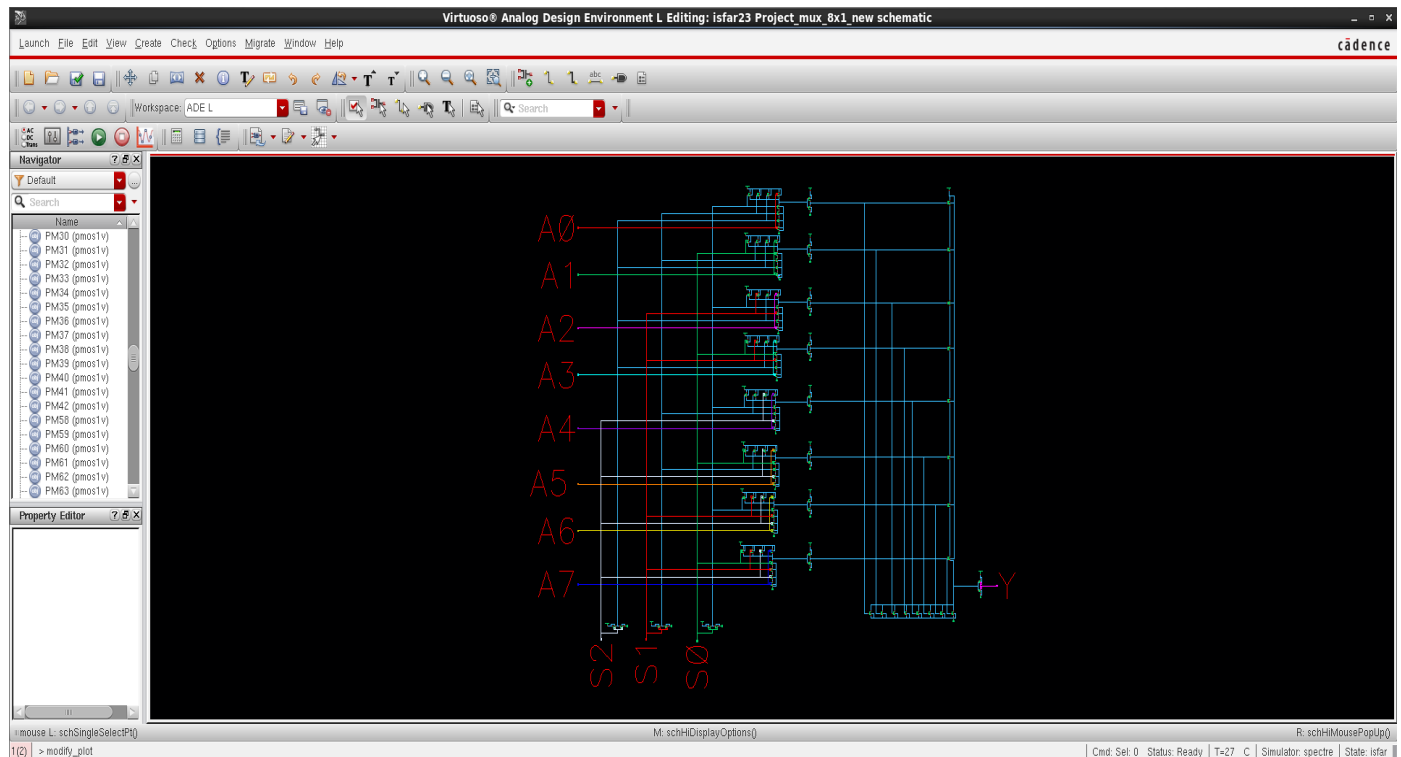


**Fig.1:** Schematic of 8x1 MUX
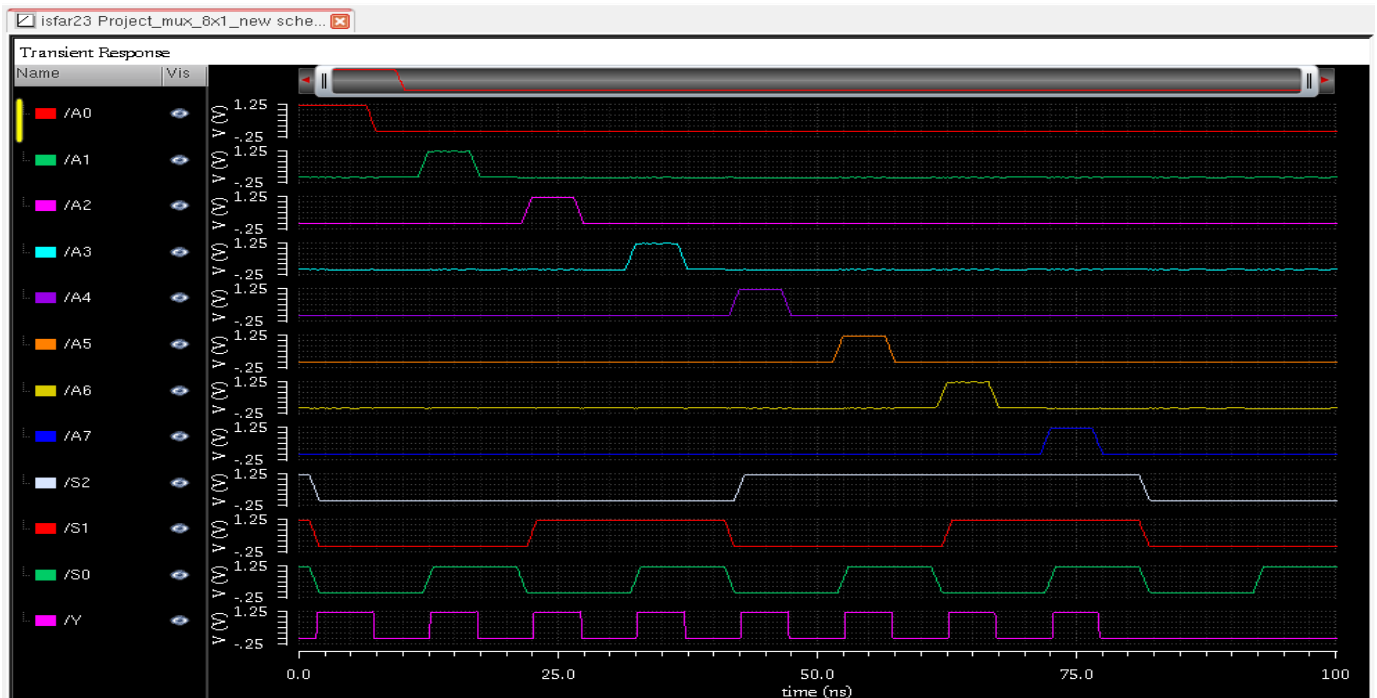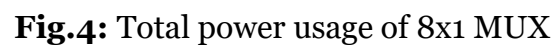
## ADE Simulations:




**Fig.2:** ADE simulation of 8x1 MUX

**Fig.3:** Waveform of power usage of 8x1 MUX




## Symbol:

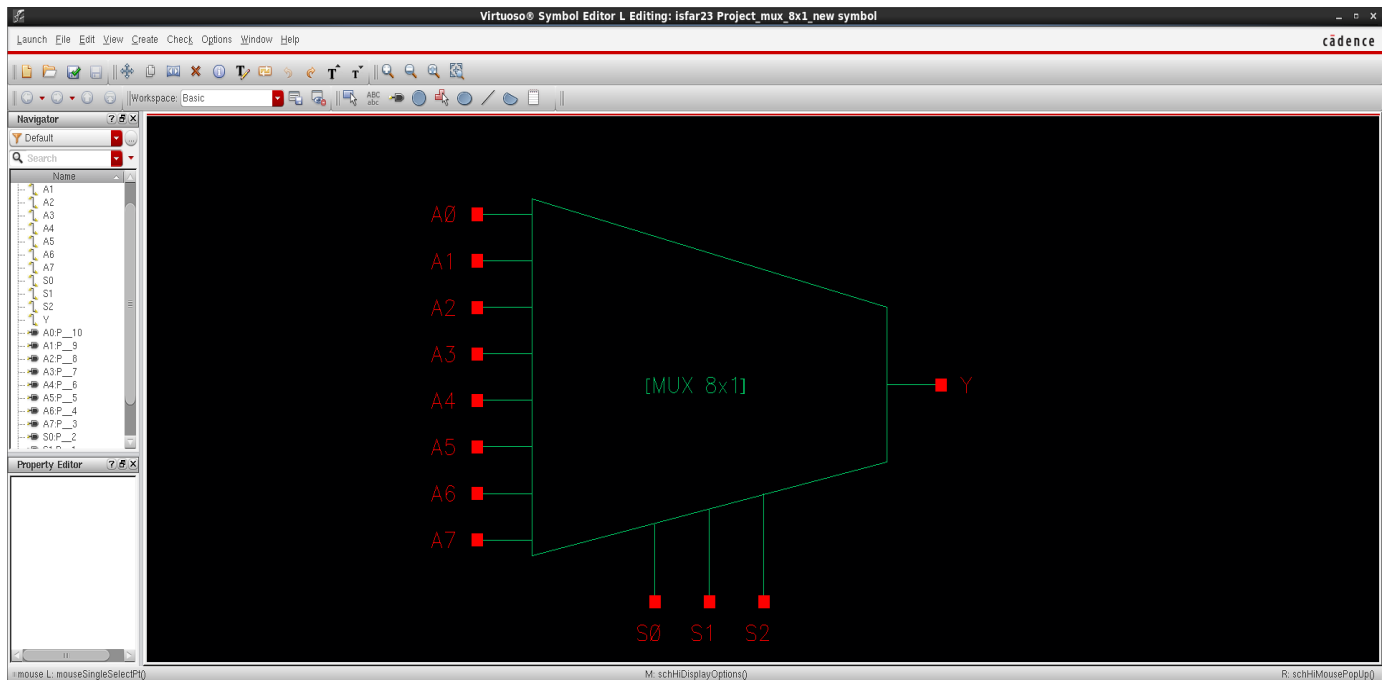

**Fig.5:** ADE simulation of 8x1 MUX

## Stick Diagram:

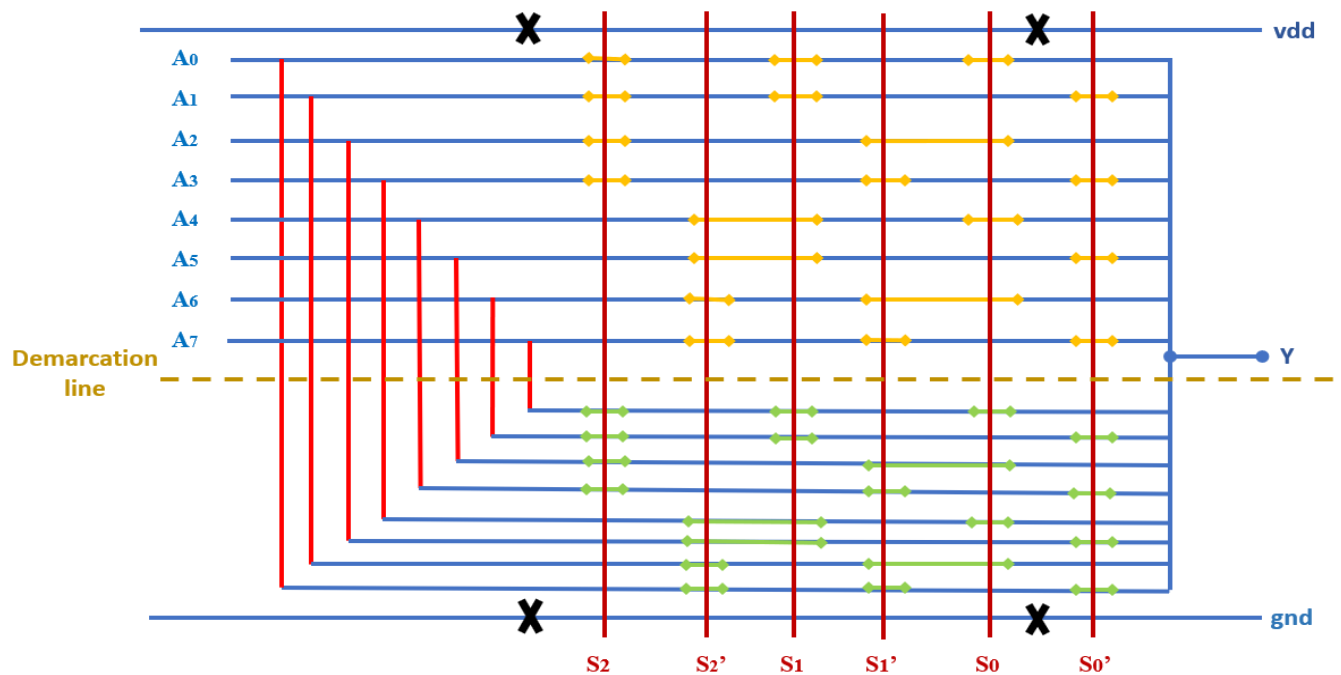

**Fig.6:** Stick diagram of 8x1 MUX